



**VIT**Vellore Institute of Technology  
(Deemed to be University under section 3 of UGC Act, 1956)

Reg. No.:


Name:

**Continuous Assessment Test - 2 (CAT 2) – December 2022**

Programme	: <b>B.Tech.</b>	Semester	: <b>FALL 2022 – '23</b>
Course	: <b>Basic Electrical and Electronics Engineering</b>	Code	: <b>BEEE102L</b>
Faculty	: <b>Dr. D. R. Binu Ben Jose Dr. S. Kuruseelan Prof. AN. Abhirami Dr. P. Sri Ramalakshmi Prof. V. Ananthakrishnan Dr. K. Iyswarya Annaporani Dr. Rupa Mishra Dr. D. Subbulekshmi Dr. G. Kanimozhi</b>	Slot	: <b>B1</b>
		Class Number	: <b>CH2022231700078 CH2022231700076 CH2022231700070 CH2022231700080 CH2022231700084 CH2022231700068 CH2022231700072 CH2022231700074 CH2022231700082</b>
Time	: <b>1 hour, 30 minutes</b>	Max. Marks	: <b>50</b>

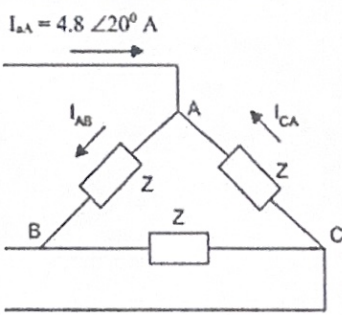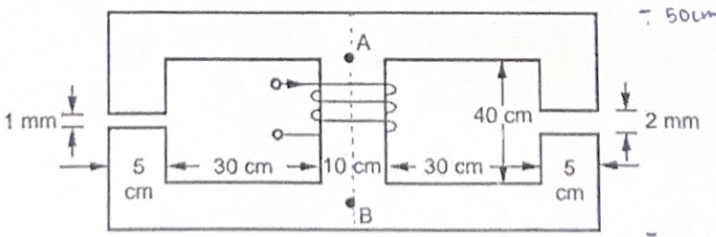Q. No.	Question Description	Marks
1.	<p>In a simple three phase balanced 3 wire system, the phase sequence is abc and the source voltage is <math>V_{AB} = 120\angle 30^\circ</math> V (lead by <math>30^\circ</math>). The supply is connected to a three phase delta load. If the line current is <math>4.8\angle 20^\circ</math> A (lead by <math>20^\circ</math>), find the power factor and the per phase resistance and reactance of the delta load.</p> 	10
2.	<p>For the magnetic circuit shown below has a coil of 1000 turns with the core thickness of 5 cm and exciting current of 0.5 A. Find the flux density and flux in each of the outer limbs and the central limb. Assume the relative permeability for iron of the core to be infinity (<math>\infty</math>).</p> 	10

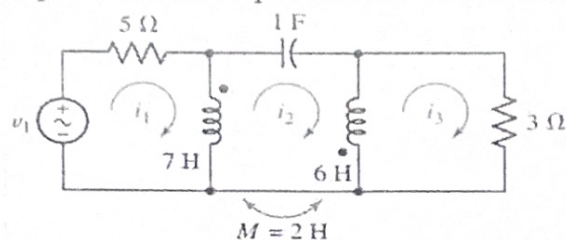3. Write a complete set of phasor mesh equations for the circuit shown below



10

4. Simplify the expression

i.  $Y = \bar{A}B + ABD + A\bar{B}\bar{C}\bar{D} + BC$

ii.  $f = \bar{x}\bar{z} + y\bar{z} + \bar{y}\bar{z} + xyz$

iii.  $f = \bar{A}B + AB + A\bar{B}$

10

5. a. Using K-map, minimize the function  $F(A, B, C, D)$  given in SOP representation.  
b. Draw a logic diagram for the reduced function using basic gates.

$F(A, B, C, D) = \Sigma(2, 5, 7, 8, 10, 12, 13, 15).$

10