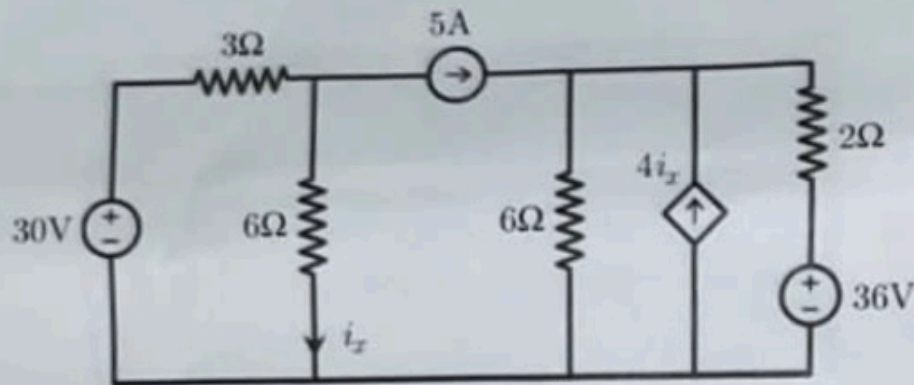


Final Assessment Test (FAT) – January/February 2023


Programme	B.Tech.	Semester	Fall Semester 2022-23
Course Title	BASIC ELECTRICAL AND ELECTRONICS ENGINEERING	Course Code	BEEE102L
Faculty Name	Prof. MOHAMMED ANEESH Y	Slot	E1+TE1
		Class Nbr	CH2022231700047
Time	3 Hours	Max. Marks	100

Part - A (10 X 10 Marks)
Answer All questions

1. Find current, i_x and the power supplied by the current dependent current source for the circuit shown in Figure. [10]




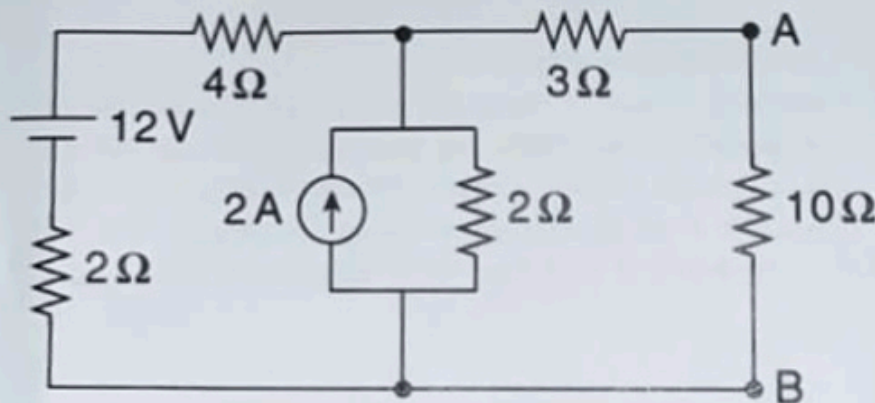2. Calculate the current flowing through the load resistor (R_L), $10\ \Omega$ connected across AB in the circuit given below using Thevenin's theorem. Find the value of R_L for maximum power transfer and also the maximum power which can be supplied at AB. [10]




3. A series RLC circuit is connected across a voltage source, $v(t) = 12\sin(2t+30^\circ)$ as shown in Figure. [10]
- a) Find impedance, power factor, power supplied by the source and the voltage across the capacitor.

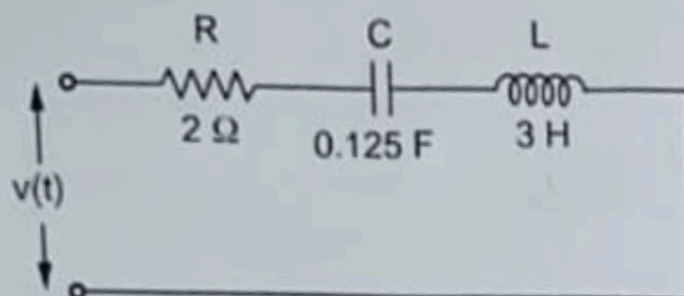b) Write the time domain equations for current and voltage across the inductor.



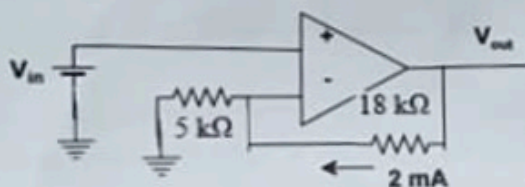4. A three phase star connected supply with abc phase sequence having phase voltage, $V_{an} = 230 \angle 0^\circ$ V (rms) is supplying a balanced delta connected load. The load draws 5 kW power per phase at 0.8 power factor lagging. Find the line currents and the currents in each phase of the load. What is the load impedance per phase? [10]
5. a) Implement the following Boolean function with 8 X 1 multiplexer. Use x, y, z as select inputs for the multiplexer. [10]
 $f(x, y, z, w) = \sum m(0, 2, 3, 5, 6, 7, 8, 10, 11)$
 b) Obtain the minimal SOP expression for 'f' using K- Map and implement the same using logic gates.
6. The induced emf in a DC machine while running at 750 rpm is 220 V. Calculate [10]
 a) the speed at which the induced emf is 250 V by assuming constant flux.
 b) the percentage increase in field flux for an induced emf of 250 V and speed of 700 rpm.
7. a) Determine the input and output voltage for the circuit given below. [10]



Handwritten notes for question 7:

$$\frac{V_{in}}{R} = \frac{V_{out}}{R}$$

$$\frac{V_{in}}{5k} = \frac{V_{out}}{18k}$$

$$V_{out} = \frac{18}{5} V_{in} = 3.6 V_{in}$$

- b) Explain the operation of a variable reluctance stepper motor.
8. A magnetic circuit made of mild steel is shown in Figure. The central limb is wound with 500 turns and has a cross sectional area of 800 mm^2 . Each of the outer limbs has a cross sectional area of 500 mm^2 . The air gap has a length of 1 mm. Calculate the current required to set up a flux of 1.3 mWb in the central limb assuming no magnetic leakage and fringing. Mild steel required 3800 AT/m to produce flux density of 1.625 T and 850 AT/m to produce flux density of 1.3 T. [10]

Handwritten calculations for question 8:


$$\phi = 1.3 \text{ mWb} = 1.3 \times 10^{-3} \text{ Wb}$$

$$B = \frac{\phi}{A} = \frac{1.3 \times 10^{-3}}{800 \times 10^{-6}} = 1.625 \text{ T}$$

$$H = \frac{B}{\mu_r \mu_0} = \frac{1.625}{1 \times 4\pi \times 10^{-7}} = 320000 \text{ AT/m}$$

$$NI = H \cdot l = 320000 \times 1 = 320000 \text{ AT}$$

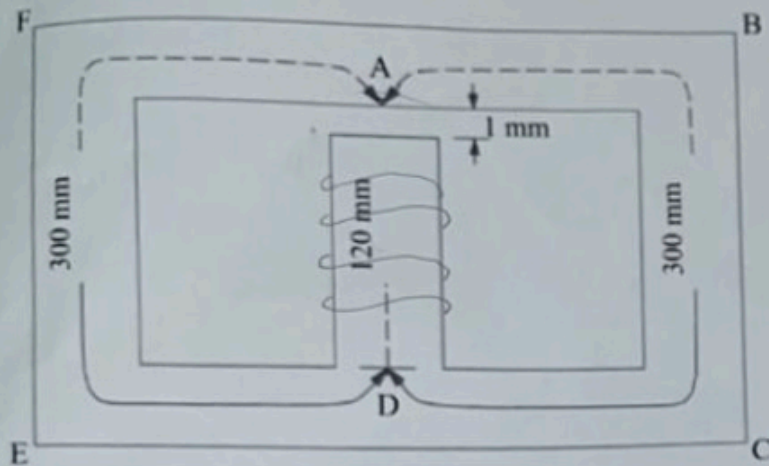
$$I = \frac{320000}{500} = 640 \text{ A}$$



[10]

9. a) Convert 10101.011_2 to i) decimal ii) octal and iii) hexadecimal format.
 b) Perform these operations by using 8-bit signed 2's-complement arithmetic and check for overflow in each case:
 (i) $15_{10} - 63_{10}$ (ii) $-17_{10} - 15_{10}$
10. a) Find the values of I and V for the circuit of Figure, assuming that the diodes are ideal.

[10]

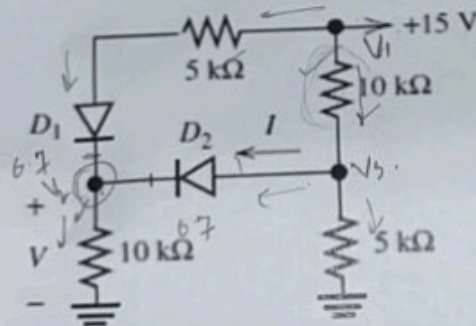

- b) What is a Zener diode? For what is it typically used? Draw the volt ampere characteristic of an ideal 5.8-V Zener diode.

