




Continuous Assessment Test(CAT) – I /II - JAN 2024


Programme	: B.Tech (ECE/ECM/EVD)	Semester	: WS 2023-24
Course Code & Course Title	: BECE102L Digital System Design	Class Number	: CH2023240501131 CH2023240501151
Faculty	: Dr A Anita Angeline & Dr A Prathiba	Slot	: D1 +TD1
Duration	: 90 Minutes	Max. Mark	: 50

General Instructions:

- Write only your registration number on the question paper in the box provided and do not write other information.
- Only non-programmable calculator without storage is permitted

Answer all questions

 Q. No	Sub Sec.	Description	Marks
1.		<p>a) For $F1 = x(\bar{y}z + yz)$, determine $\overline{F1}$.</p> <p>b) Simplify $F2 = ABCD + \bar{A}BD + AB\bar{C}D$</p> <p>c) Determine the functionality of the Static CMOS implementation depicted in Fig.1, and identify the path output for A=1; B=C=D=0</p>  <p>Fig.1</p>	[10]
2.		<p>Derive the circuit consisting only of two-input NAND gates for the function $f(x_1, x_2, x_3, x_4) = \sum m(0, 1, 2, 3, 4, 6, 8, 9, 12)$. Assume that the input variables are available in both uncomplemented and complemented forms.</p>	[10]

 3.	<p>Design the hardware depicted in Fig.2, using Verilog HDL code and write the testbench for the schematic (top module).</p>  <p style="text-align: center;">Fig.2</p>	[10]
4.	<p>a) Considering A0, A1, B0, B1 as single bit data, configure a circuit to implement $F3 = (A1+B1) + (A0+B0)$ using appropriate adders and justify your design.</p> <p>b) Considering W, X, Y, Z as single bit data, design a digital circuit to implement $F4 = \overline{W} \overline{X} \overline{Y} \overline{Z} + 1$ using appropriate gates and adder units and justify your design.</p>	[10]
5.	<p>Implement the Boolean function $F4 = \sum(0,2,5,7,11,14)$ using 8 X1 multiplexer.</p>	[10]
*****All the best *****		